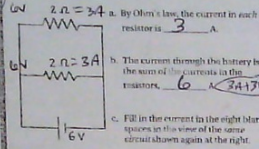



Parallel Circuits

$I = \frac{V}{R} = \frac{6V}{2\Omega} = 3A$


25 In the circuit shown below, there is a voltage drop of 6 V across each 2 Ω resistor.



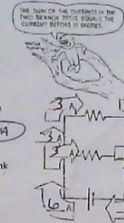- a. By Ohm's law, the current in each resistor is 3 A.
 b. The current through the battery is the sum of the currents in the resistors, 6 A.
 c. Fill in the current in the eight blank spaces in the view of the same circuit shown again at the right.



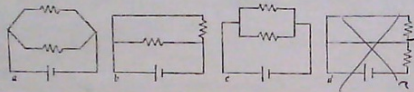26 Cross out the circuit below that is not equivalent to the circuit above.




2 resistors on same branch

V-drop same for all resistors

27 Consider the parallel circuit at the right.

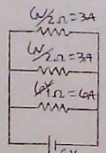- a. The voltage drop across each resistor is 6V.
 b. The current in each branch is:
 2 Ω resistor: 3 A
 2 Ω resistor: 3 A
 1 Ω resistor: 6 A
 c. The current through the battery equals the sum of the currents which equals 12 A.
 d. The equivalent resistance of the circuit equals 0.5 Ω.




THE EQUIVALENT RESISTANCE OF A PAIR OF RESISTORS IN PARALLEL IS THEIR PRODUCT DIVIDED BY THE SUM.


$R_{tot} = \frac{R_1 \cdot R_2 \cdot R_3}{R_1 + R_2 + R_3} = \frac{2 \cdot 2 \cdot 1}{2 + 2 + 1} = \frac{4}{5} = 0.8 \Omega$

Compound Circuits


28 The initial circuit below left is a compound circuit made of a combination of resistors. It is reduced to a single equivalent resistance by the three steps, one circuit to the right. In step 1, it is shown the equivalent resistance of the parallel 4 Ω resistors. In step 2, combine this in series with the 1 Ω resistor. In step 3, combine the two parallel paths to obtain the equivalent resistance of the circuit. (Note the similarity of this circuit and Figure 35-19 in your textbook.)

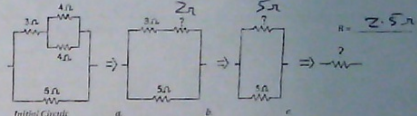

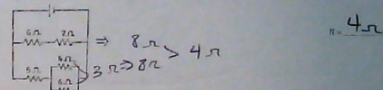29 The circuit below is similar to Figure 35-11 in your textbook. In three successive steps, as in Question 4, replace each pair of resistors by a single resistor of equivalent resistance.



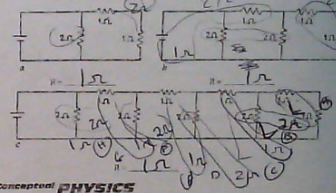30 Find the equivalent resistance of these three circuits.



$R_{tot} = \frac{1}{\frac{1}{2} + \frac{1}{2} + 1} = 0.5 + 0.5 + 1 = 2 \Omega$

Parallel
 tot resistance = less than each resistor
 - 1/2 in pairs than 1/2 value
 3 1 resistor
 current = sum of all branches